

## Computer-Aided VLSI System Design

### Homework 2: Simple RISC-V CPU

TA: 顏子茗 r13943119@ntu.edu.tw **Due Tuesday, Oct. 14, 13:59**

TA: 陳柏任 d13943013@ntu.edu.tw

### Data Preparation

- Decompress 1141\_hw2.tar with following command


```
tar -xvf 1141_hw2.tar
```

Folder	File	Description
00_TB	data_mem.vp	Module of memory (protected)
	define.v	File of definition
	testbed_temp.v	Testbench template
00_TB / PATTERN/p*	inst.dat	Pattern of instruction in binary format
	inst_assembly.dat	Corresponding assembly code of the instruction pattern
	data.dat	Pattern of final data in memory
	status.dat	Pattern of corresponding status
01_RTL	core.v	Your design
	rtl.f	File list
	01_run	VCS command for simulation
	99_clean_up	Command to clean temporary data


### Introduction

Central Processing Unit (CPU) is the important core in the computer system. In this homework, you are asked to design a simple RISC-V CPU, which contains the basic module of program counter, ALU and register files. The instruction set of the simple CPU is similar to RISC-V structure. Since the files of testbench (testbed.v) are either protected or not provided, you also need to design the testbench to test your design.

Instruction set

 

## Block Diagram

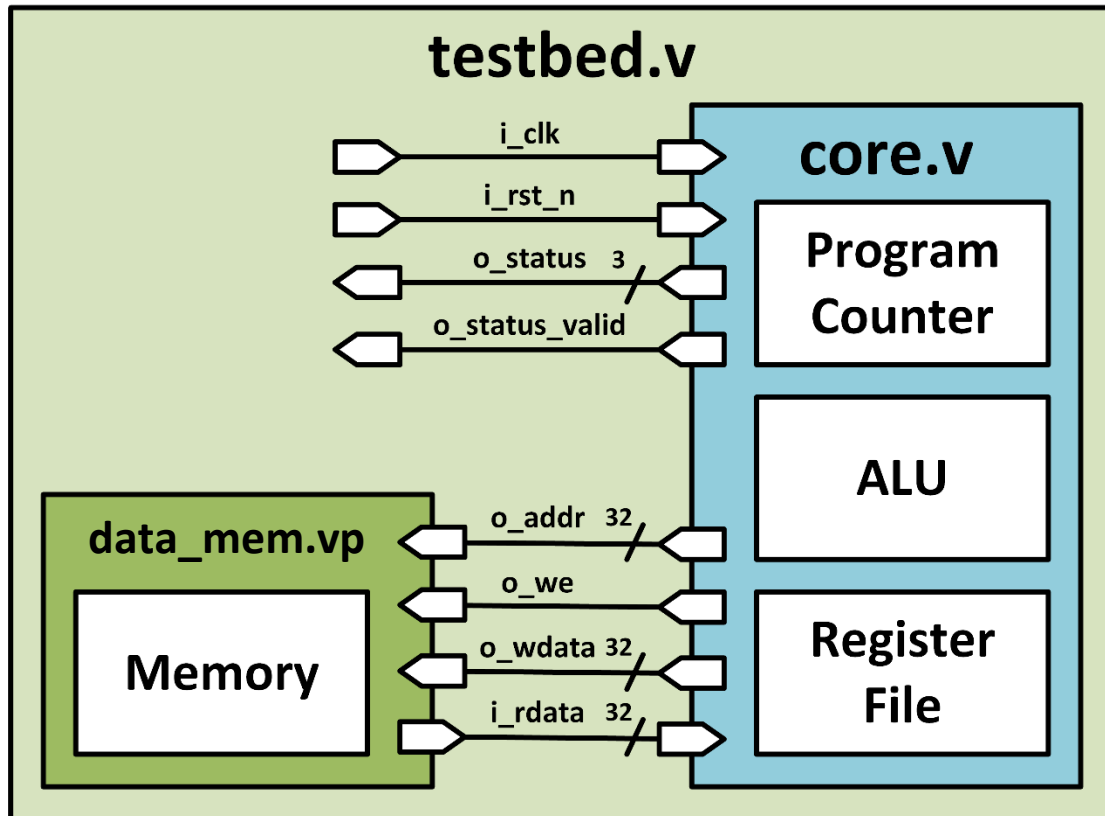

## Specifications

1. Top module name: core
2. Input/output description:

Signal Name	I/O	Width	Simple Description
i_clk	I	1	Clock signal in the system.
i_rst_n	I	1	Active <b>low</b> asynchronous reset.
o_we	O	1	Write enable of memory Set <b>low</b> for reading mode, and <b>high</b> for writing mode
o_addr	O	32	Address for memory
o_wdata	O	32	Data input to memory
i_rdata	I	32	Data or instruction output from memory
o_status	O	3	Status of core processing to each instruction
o_status_valid	O	1	Set <b>high</b> if ready to output status


3. All outputs should be synchronized at clock **rising** edge.
4. You should set all your **outputs** and **register file** to be **zero** when i\_rst\_n is **low**. Active low asynchronous reset is used.

5. Memory is provided. All values in memory are reset to be zero.
6. You should create **32 signed 32-bit registers** and **32 single-precision floating - point registers** in register file.
7. To load data or instruction from the memory, set o\_we to **0** and o\_addr to relative address value. i\_rdata can be received at the next rising edge of the clock.
8. To save data to the memory, set o\_we to **1**, o\_addr to relative address value, and o\_wdata to the written data.
9. Your o\_status\_valid should be turned to **high** for only **one cycle** for every o\_status.
10. The testbench will get your output at negative clock edge to check the o\_status if your o\_status\_valid is **high**.
11. When you set o\_status\_valid to **high** and o\_status to **6**, stop processing. The testbench will check your memory value with golden data.
12. If invalid operation happened, stop processing and raise o\_status\_valid to **high** and set o\_status to **5**. The testbench will check your memory value with golden data.
13. **Less than 1024** instructions are provided for each pattern.
14. The whole processing time can't exceed **120000** cycles for each pattern.

## Design Description

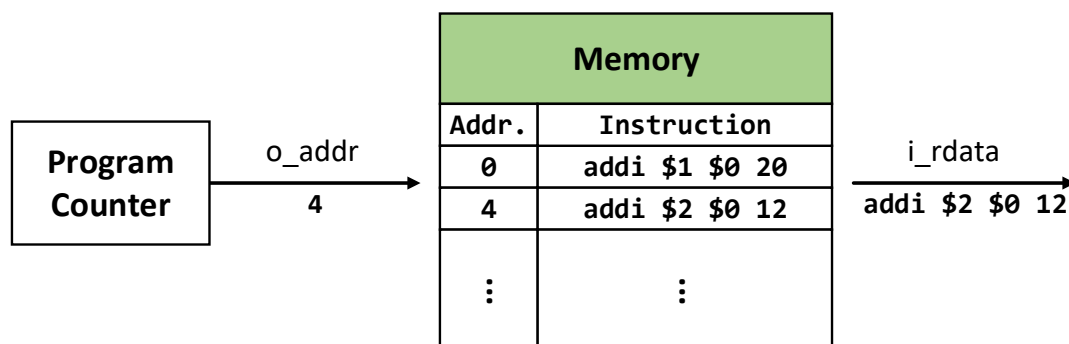1. Program counter is used to control the address of memory for instruction.

$\$pc = \$pc + 4$  for every instruction (except **beq**, **blt**, **jalr**)



2. Register file contains 32 signed 32-bit registers and 32 single-precision floating - point registers for operation.
3. Instruction mapping
  - a. **R-type**

[31:25]	[24:20]	[19:15]	[14:12]	[11:7]	[6:0]
funct7	r2/f2	r1/f1	funct3	rd/fd	opcode

## b. I-type

[31:20]	[19:15]	[14:12]	[11:7]	[6:0]
imm[11:0]	r1/f1	funct3	rd/fd	opcode

## c. S-type

[31:25]	[24:20]	[19:15]	[14:12]	[11:7]	[6:0]
imm[11:5]	r2/f2	r1/f1	funct3	imm[4:0]	opcode

## d. B-type

[31]	[30:25]	[24:20]	[19:15]	[14:12]	[11:8]	[7]	[6:0]
imm[12]	imm[10:5]	r2/f2	r1/f1	funct3	imm[4:1]	imm[11]	opcode

## e. U-type

[31:12]	[11:7]	[6:0]
imm[31:12]	rd/fd	opcode

## f. EOF

[31:7]	[6:0]
Not used	opcode

4. The followings are the instructions you need to design for this homework:

Operation	Assemble	Type	Meaning	Note
Subtract	sub	R	$\$rd = \$r1 - \$r2$	Signed Operation
Add immediate	addi	I	$\$rd = \$r1 + im$	Signed Operation
Load word	lw	I	$\$rd = Mem[\$r1 + im]$	Signed Operation
Store word	sw	S	$Mem[\$r1 + im] = \$r2$	Signed Operation
Branch on equal	beq	B	if( $\$r1 == \$r2$ ), $\$pc = \$pc + im$ ; else, $\$pc = \$pc + 4$	PC-relative Signed Operation
Branch less than	blt	B	if( $\$r1 < \$r2$ ), $\$pc = \$pc + im$ ; else, $\$pc = \$pc + 4$	PC-relative Signed Operation
Jump and link register	jlr	I	$\$rd = \$pc + 4$ ; $\$pc = (\$r1 + im) \& (\sim 0x1)$	PC-relative Signed Operation
Add upper immediate to PC	auipc	U	$\$rd = \$pc + (im \ll 12)$	PC-relative Signed Operation
Set on less than	slt	R	if( $\$r1 < \$r2$ ), $\$rd = 1$ ; else, $\$rd = 0$	Signed Operation
Shift right logical	srl	R	$\$rd = \$r1 \gg \$r2$	Unsigned Operation

Floating-point subtract	fsub	R	$\$fd = \$f1 - \$f2$	Floating-point Operation
Floating-point multiply	fmul	R	$\$fd = \$f1 * \$f2$	Floating-point Operation
Floating-point to signed integer conversion	fcvt.w.s	R	$\$rd = s32f32(\$f1)$	Floating-point Operation
Load floating-point	flw	I	$\$fd = \text{Mem}[\$r1 + im]$	Signed Operation
Store floating-point	fsw	S	$\text{Mem}[\$r1 + im] = \$f2$	Signed Operation
Floating-point classify	fclass	R	$\$rd = \text{fclass}(\$f1)$	Classify floating-point format
End of File	eof	EOF	Stop processing	Last instruction in the pattern

Note: The notation of **im** in instruction is **2's complement**.

Note: The \$r notes that the data is read/written to integer register file; the \$f notes that the data is read/written to floating-point register file.

Note: Set the result of fsub and fmul to +0 if the arithmetic result is 0

5. Interface of memory (size: 2048×32 bit)

- i\_addr[12:2] for address mapping in memory
- Instructions are stored in address 0 - address 4095
- Data are should be write to address 4096 - address 8191
- To fetch data of memory in your testbench, use following instance name

```
u_data_mem.mem_r[i]
```

```
module data_mem (
    input        i_clk,
    input        i_rst_n,
    input        i_we,
    input [ 31 : 0 ] i_addr,
    input [ 31 : 0 ] i_wdata,
    output [ 31 : 0 ] o_rdata
);
```

6. Invalid operation may be happened.

- **Situation1**: Overflow happened at integer arithmetic instructions (**sub**, **addi**)

- **Situation2:** Infinite, NaN happened at floating-point arithmetic instructions (**fsub**, **fmul**, **fcvt.w.s**)
  - For **fcvt.w.s** instruction, additional consideration is required when the floating-point value being converted to a 32-bit signed integer exceeds the representable range of a 32-bit signed integer
  - Do not consider when loading/storing infinite or NaN numbers from memory
  - Do not consider when executing **fclass** on infinite or NaN numbers
- **Situation3:** Overflow and underflow result happened at floating-point arithmetic instructions (**fsub**, **fmul**)
  - Consider the overflow and underflow before rounding arithmetic result
  - Underflow does not include zero
- **Situation4:** If output address are mapped to unknown address in memory.
  - Consider the case when an instruction is trying to load/store the address of memory for instruction
  - Consider the case when program counter is fetching instruction from the address of memory for data
  - Do not consider the case if instruction address is beyond eof, but the address mapping is in the size of memory for instruction

7. 7 statuses of o\_status

<b>o_status</b>	<b>Definition</b>
3'd0	R_TYPE_SUCCESS
3'd1	I_TYPE_SUCCESS
3'd2	S_TYPE_SUCCESS
3'd3	B_TYPE_SUCCESS
3'd4	U_TYPE_SUCCESS
3'd5	INVALID_TYPE
3'd6	EOF_TYPE


8. Last instruction would be **eof** for every pattern.

9. There is no unknown opcode in the pattern.


## Sample Waveform

---


1. Status check
  - a. End of file (eof)

 

b. Invalid operation

 

2. Memory interface

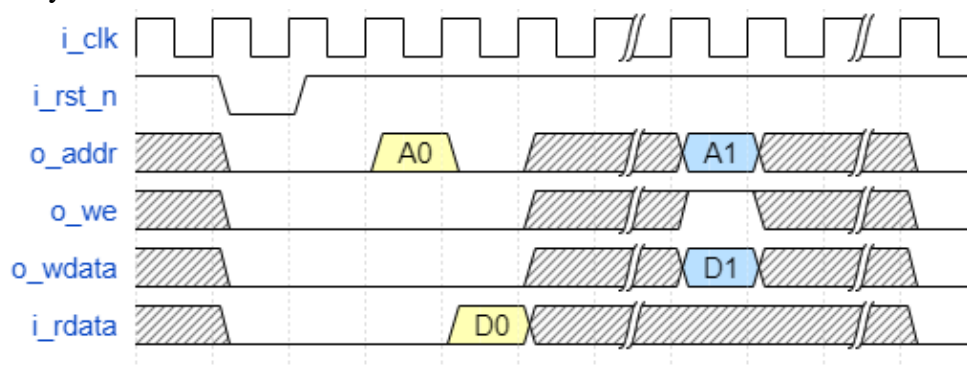

## Testbed

1. Things to add in your testbench

- Clock
- Reset
- Waveform file (.fsdb)
- Function test
- ...

## Submission

2. Create a folder named **studentID\_hw2**, and put all below files into the folder

```
r13943119_hw2/
├── 01_RTL
│   ├── core.v
│   ├── rtl.f
│   └── (other design files)
```

Note: Use **lower case** for the letter in your student ID. (Ex. r13943119\_hw2)

3. Compress the folder **studentID\_hw2** in a **tar file** named **studentID\_hw2\_vk.tar** (**k is the number of version,  $k=1,2,\dots$** )

```
tar -cvf studentID_hw2_vk.tar studentID_hw2
```

TA will only check the last version of your homework.

**Note: Use **lower case** for the letter in your student ID. (Ex. r13943119\_hw2\_v1)**

**Note: Pack the folder on IC Design LAB server to avoid OS related problems.**

4. Submit to NTU Cool

## Grading Policy

1. TA will run your code with following format of command. Make sure to run this command with no error message. [p0–p3 (p0 shown as example below)]

```
vcs -f rtl.f -full64 -R -sverilog -debug_access+all +define+p0 -v2k
```

2. Pass the patterns to get full score.
  - Provided pattern: **70%** (patterns: 4)
    - **15%** for each pattern
    - **10%** for spyglass check (lint\_rtl and lint\_rtl\_enhanced)
    - **Don't implement the answers in your design directly!**
  - Hidden pattern: **30%**
    - **20 patterns** in total
3. Delay submission
  - **No delay submission is allowed**
  - Lose **5 point** for any wrong naming rule. Don't compress all homework folder.

## Hint

1. Design your FSM with following states
  - Idle
  - Instruction Fetching
  - Instruction decoding
  - ALU computing/ Load data
  - Data write-back
  - Next PC generation
  - Process end

## Reference

- [1] RISC-V User Manual
  - <https://riscv.org/wp-content/uploads/2017/05/riscv-spec-v2.2.pdf>
- [2] IEEE 754 Single Precision Format
  - [https://zh.wikipedia.org/zh-tw/IEEE\\_754](https://zh.wikipedia.org/zh-tw/IEEE_754)
- [3] Round to Nearest Even



- <https://www.cs.cmu.edu/afs/cs/academic/class/15213-s16/www/lectures/04-float.pdf>
- [4] F Standard Extension for Single-Precision Floating-Point
- <https://five-embeddev.com/riscv-user-isa-manual/Priv-v1.12/f.html>